

015-0282-00 Levelling
Head Substitute for
the Tektronix SG504

Introduction

The Tektronix SG504 is a levelled sine wave generator that covers the frequency range 245MHz to 1050MHz in two bands. It uses an external levelling head part number 015-0282-00. The SG504 is frequently seen for sale, but more often than not without the necessary levelling head. The levelling heads very rarely appear for sale, and often command very high prices or don't work properly.

I decided that there must be a market for a kit to replace the “guts” of a failed levelling head, or to allow a complete replacement to be constructed using a suitable housing.

I therefore completely disassembled a failed levelling head and reverse engineered the circuit. The original levelling head was constructed partially on standard fibreglass PCB substrate, and partially on a 40 mil thick hybrid, as may be seen from the photograph below:



The basic design is an RF power splitter, and a voltage doubler peak detector. The diodes for the detector are under the pink isothermal cover at the top right of the hybrid, as are the reference diodes and a few other components.


As I don't have access to a hybrid fabrication plant, I decided that I would design the replacement PCB using surface mount components on a double sided 0.8mm thick PCB. The only concern was whether standard FR4 substrate would do the

job, or whether it would be necessary to use an “exotic” (read expensive) substrate like Rogers 4350B. Extensive RF simulation of the crucial parts of the PCB design using Ansoft Designer SV indicated that there should not be a problem with using FR4.

The obvious choice for the detector diodes seemed the Avago Technologies HSMS-282x range. I eventually decided to use the uncommitted Ring Quad HSMS-282R, as this would ensure better thermal tracking between the reference diode pair and the detector diode pair. A possible alternative would have been to use two HSMS-282K, or two HSMS-282C, but the latter offered no advantage and used more board space, while for the power levels involved (-1dBm to +19dBm), the balance seemed to favour the use of the HSMS-282R. This was confirmed by Avago Technologies technical support.

Construction Notes

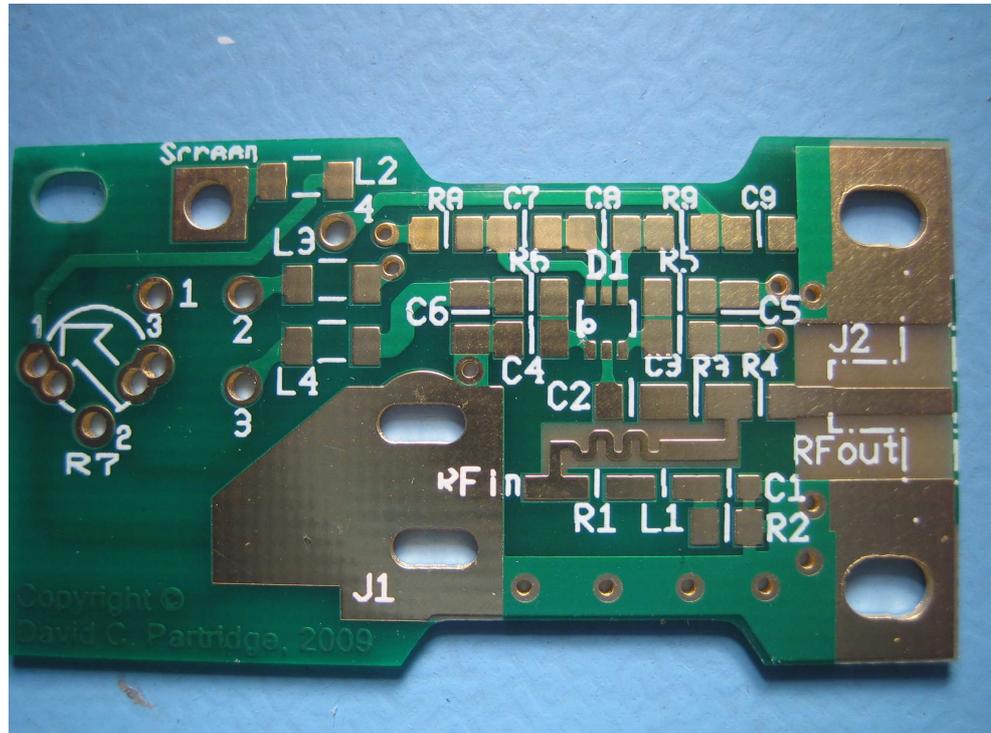Apart from a collection of parts, you will have a PCB. Here is what the PCB you get looks like:



The PCB is designed to be used either in your own case; or in the original Tektronix housing (if you have a dead levelling head). To use it in your own case I have provided pads for an SMA bulkhead end launcher at the right hand side. In this case, as well as the SMA end launcher you will need an SMA male to BNC male adapter.

If you are going to use this in the original Tektronix levelling head housing, you will need to cut out the area that is partially marked in silk screen on the RHS of the PCB. My apologies it is not as clearly marked as intended, the fabrication plant decided they didn't like silk-screen on bare copper and removed the dashes, but thankfully left the dots!


The parts kit only contains the PCB, the surface mount components, some of which were fairly hard to source (in the UK at least), and the 1kOhm trim-pot (R7). It does not include cables or connectors. A suitable Lemo connector is the FFA.0S.304.CLAC42 or FFA.0S.304.CLAC44. You can buy the latter from RS Components in the UK <http://uk.rs-online.com/web/p/circular/1732039/>

To construct the board, you'll need a fine tipped soldering iron, some very fine solder, and liquid SMT rework flux. I strongly suggest that you install the detector diode first, and work out from there. It doesn't matter which way round the detector diode is mounted by the way, which helps a lot as pin one isn't marked!

You may find it advantageous to use a very small dab of acrylic PCB lacquer to secure the diode and 0603 sized parts before soldering them. If you haven't any previous experience of SMT soldering I suggest you look at the video tutorial entitled Surface Mount Soldering 101 which you will find at:

[http://www.curiousinventor.com/guides/Surface Mount Soldering/101](http://www.curiousinventor.com/guides/Surface_Mount_Soldering/101)

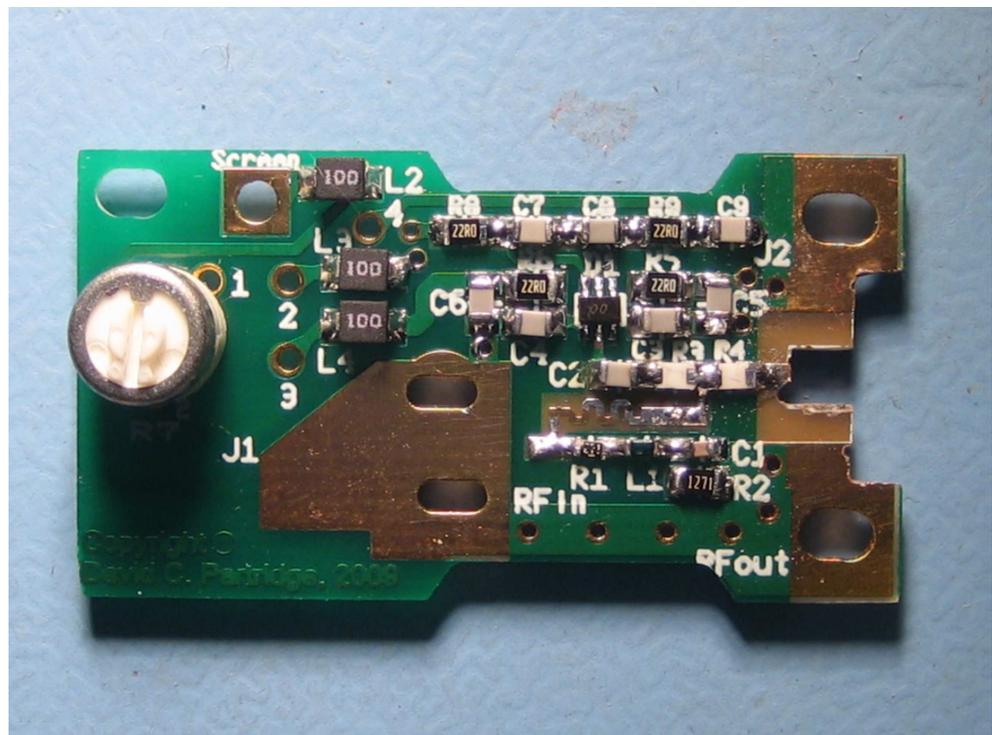Here's what the prototype board looked like with all the components installed and the cut-out for mounting in the original Tektronix housing:




I hope you make a tidier job of the cut-out than I did!


You should notice that the 50 Ohm (strictly 49.9 Ohm) resistors R3 and R4 which make up the power splitter are mounted face down. This was done deliberately to minimise stray inductance.


Mounting the PCB in the Original Housing

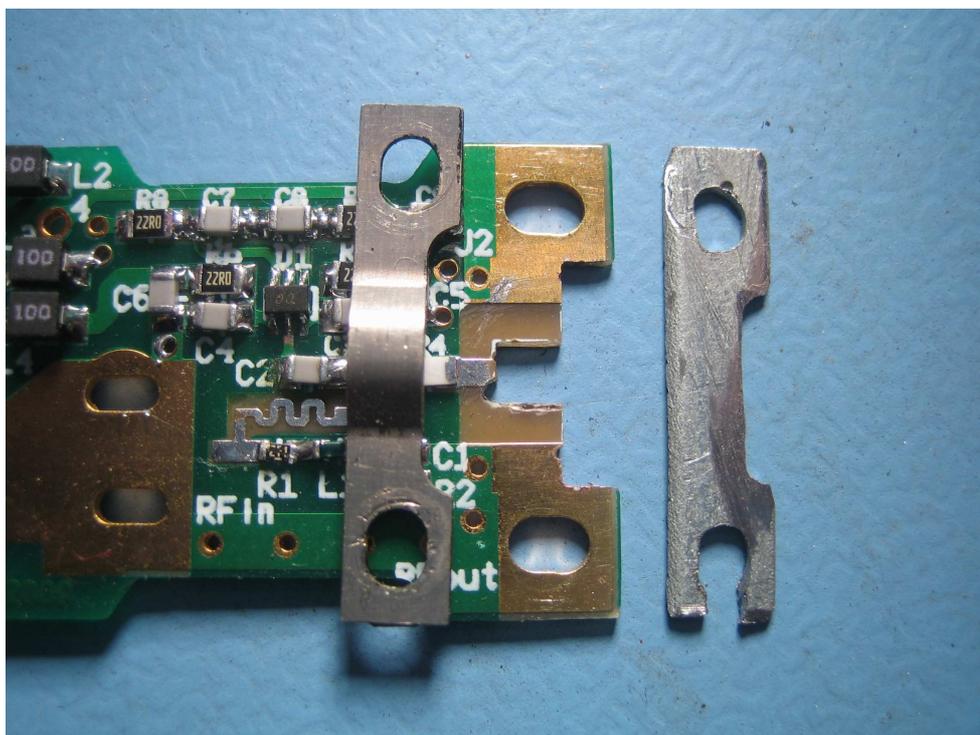To mount the head in the original housing you'll need to do two things – one is to slightly flatten the bridge section of the clamp that goes over the BNC output connector because the replacement PCB is slightly thinner than the hybrid that is mounted on the original PCB. You will also need to make up a flat metal clamp piece to go underneath it:



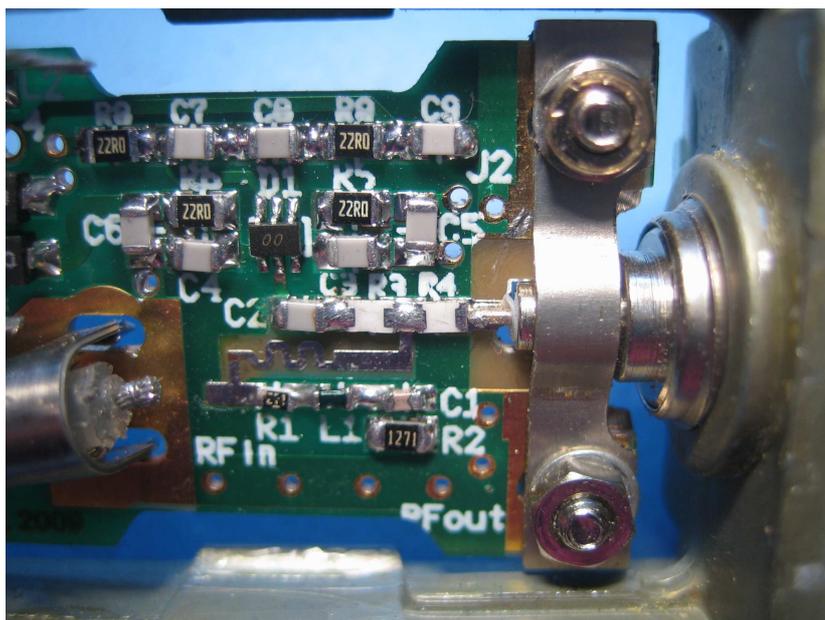
Once that is done, you can mount the PCB in the housing:



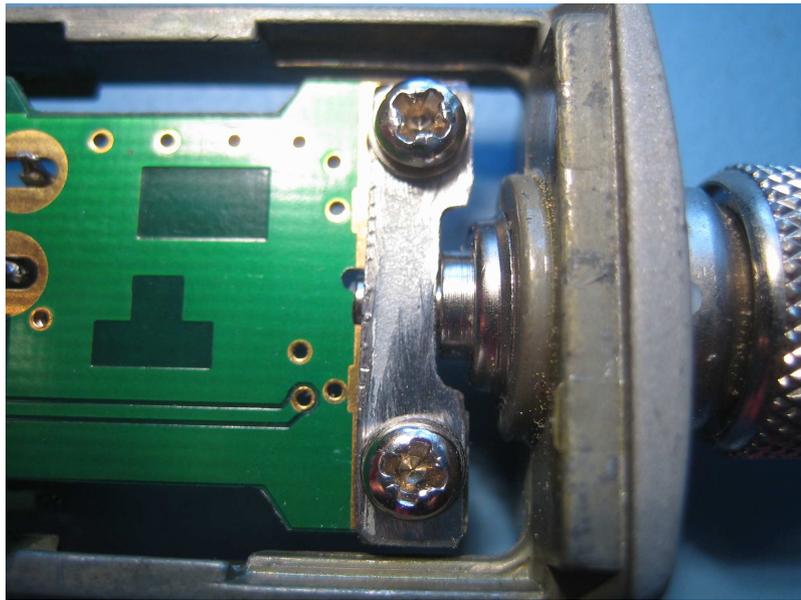

All that remains is to connect the 4 core cable to connection points 1 to 4, solder the input coax screen and use a fine wire to connect the centre core of the input coax to the pad next to R1, and finally to solder the centre connector of the output connector:


And here's the finished product:

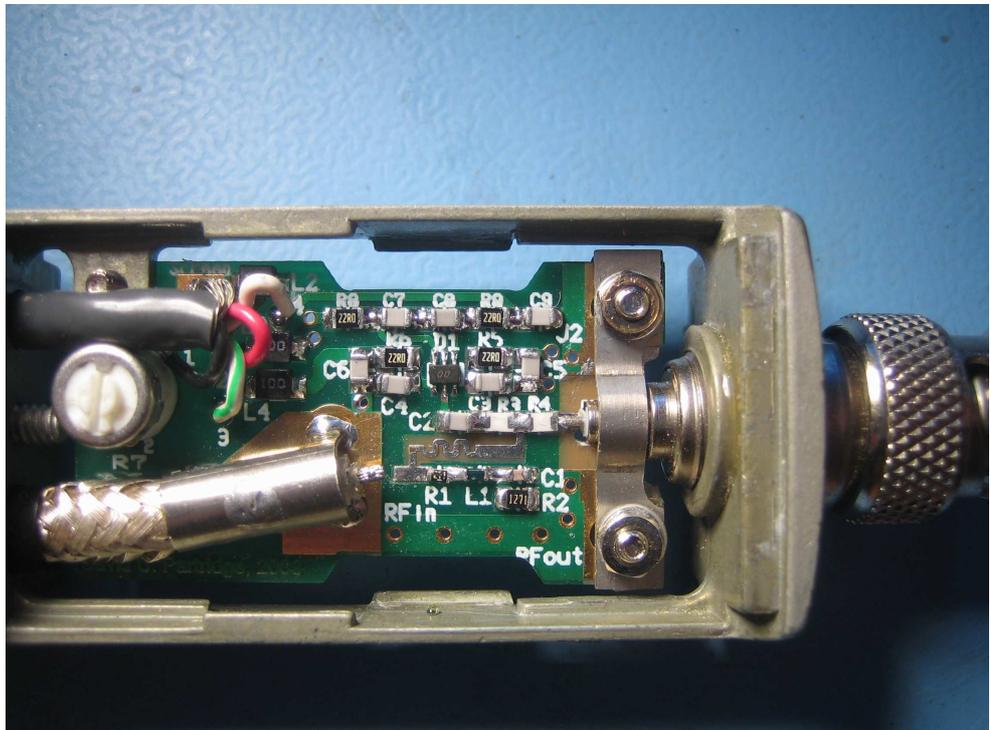

Calibrating the head

The trim-pot (R7) is used to calibrate the head for mismatches between the detector and reference diodes. In theory the HSMS-282R diodes are sufficiently well matched that I could have substituted a pair of 510 resistors for the trim-pot, but I decided to retain the same design in this respect as the original levelling head. The calibration circuit is quite simple, and the schematic is at the end of the document. I made it up on a piece of stripboard.

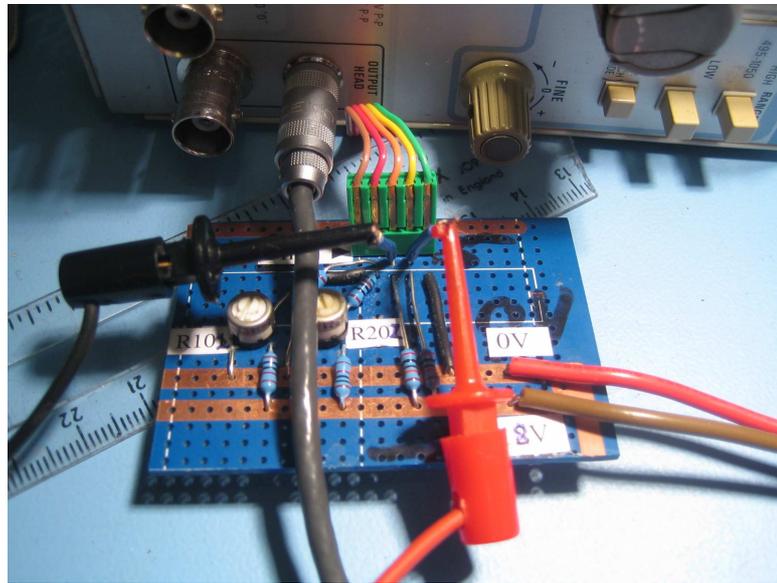The way I connected the calibrator to the head was to plug the head into the SG504, and carefully bring out the ribbon cable and five way connector from the SG504 to the five way header on the calibrator board:



The first thing you will need to do is connect the calibrator to a lab PSU set for 18.00V (make sure you get the polarity the correct way round). Then there is a “one time action” to calibrate the calibrator which involves adjusting R102 and R202 as described on the schematic page.


Once you’ve done that, you connect your voltmeter as shown and adjust R7 in the levelling head for lowest possible voltage between pin 3 and pin 4 (<1mV or better).

Once you’ve put the SG504 back together, there is a final step that needs to be taken. You must re-adjust R280 and R270 in the SG504 according to the instructions in **Step 7 Adjust Reference Amplitude at 0.05MHz** on page 3-6 of the SG504 manual. You should also check that the 6MHz output levels are correct.

¹ Do be very careful doing this – I know to my cost how easy it is to break the wires at the back of the Lemo connector.


Flatness results with the prototype head:

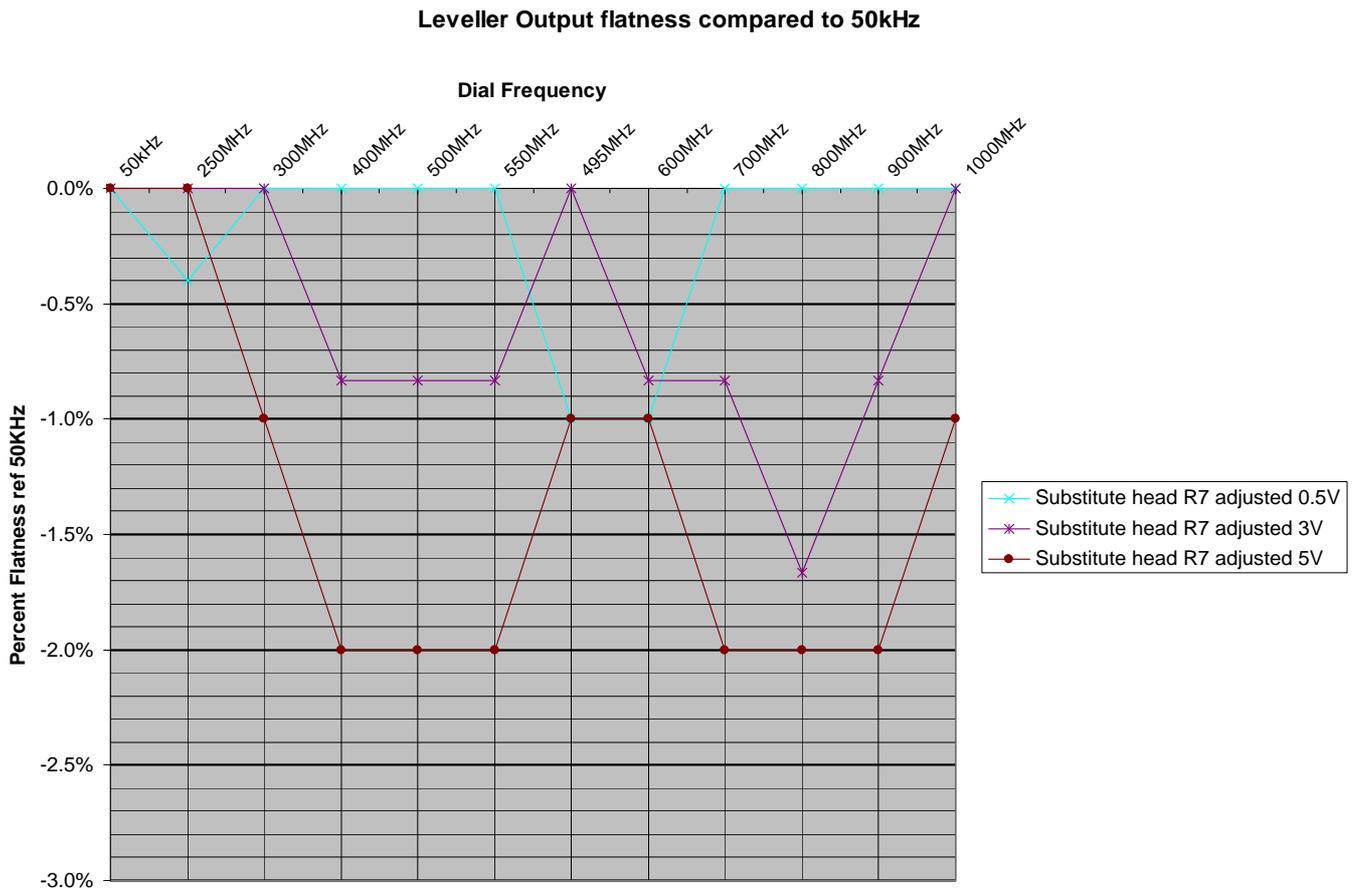Here is the graph of checking the output of the SG504 with the substitute head at three different output levels across the entire band of the SG504:



As you can see the worst case deviation of the output is [+0%, -2%] which is within the specifications of [+3%, -3%] as set by Tektronix, and only very marginally less good than my original head after I had adjusted the trim-pot.

Schematics

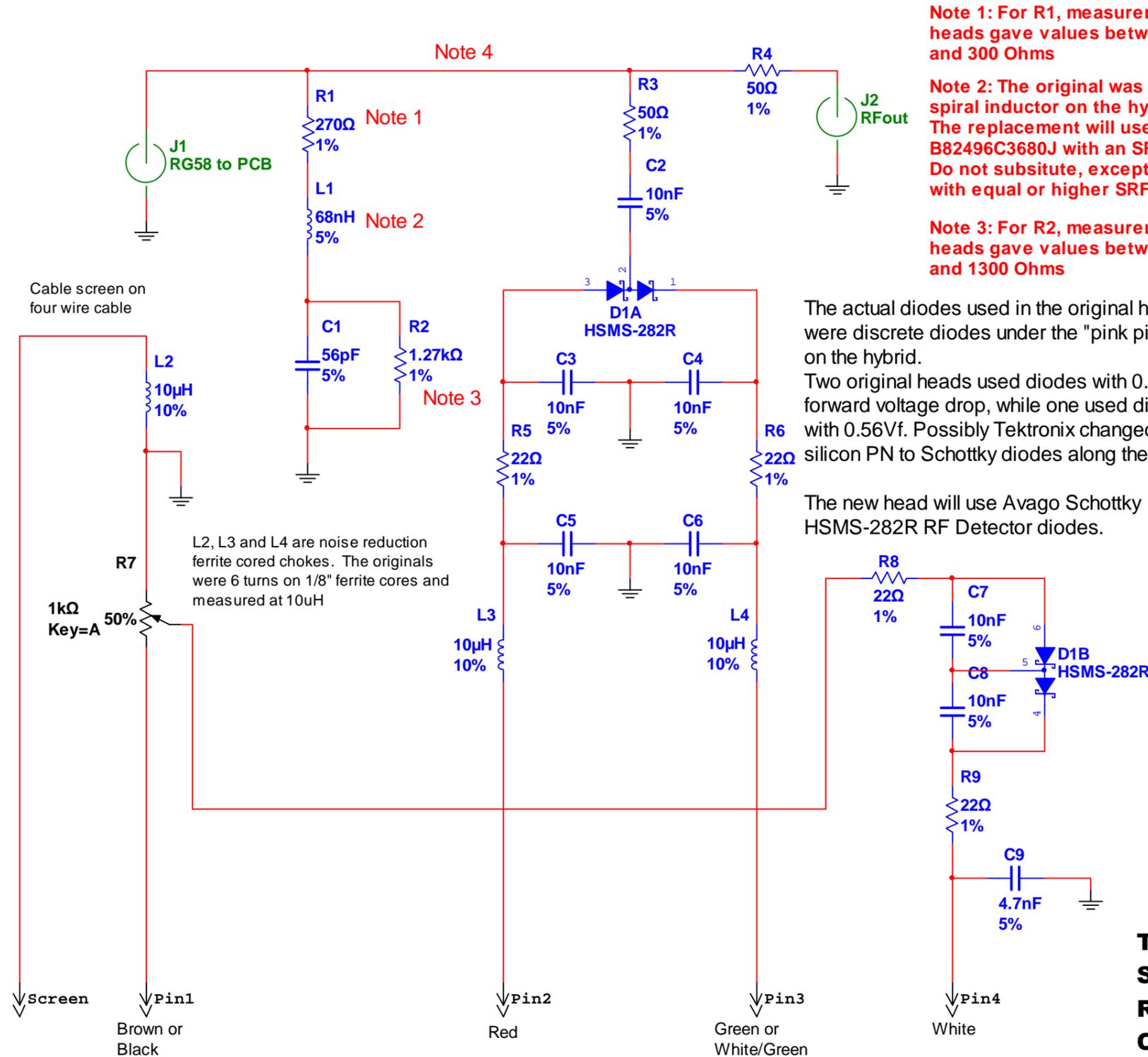

Note 1: For R1, measurements on 3 heads gave values between 240 and 300 Ohms

Note 2: The original was a rectangular spiral inductor on the hybrid of about 65nH. The replacement will use Epcos part number B82496C3680J with an SRF of 2700MHz. Do not substitute, except with equal or higher SRF

Note 3: For R2, measurements on 3 heads gave values between 1240 and 1300 Ohms

Note 4: Connection between R1 and R3,R4 was microstrip line on the 40 mil thick alumina hybrid:
 90 degree bend W1=10 mils, W2=7.5 mils
 Step W1=5 mils, W2=70 mils
 W=20 mils, P=70 mils (68 ohms)
 90 degree bend W1=20 mils, W2=10 mils
 W=10 mils, P=30 mils (84 ohms)

The actual diodes used in the original head were discrete diodes under the "pink pill" on the hybrid. Two original heads used diodes with 0.41V forward voltage drop, while one used diodes with 0.56Vf. Possibly Tektronix changed from silicon PN to Schottky diodes along the way.


The new head will use Avago Schottky HSMS-282R RF Detector diodes.

On 0.8mm FR4 1oz. copper the sections are (ignoring the bends):
 W=20 mils, P=53 mils
 W=16 mils, P=284 mils
 W=34.5 mils, P=106 mils
 W=20 mils, P=29 mils

ALL resistors are Thin Film parts with tolerance as specified or better. Actual values used for R3, R4 will be 49.9 ohms

ALL capacitors are C0G type

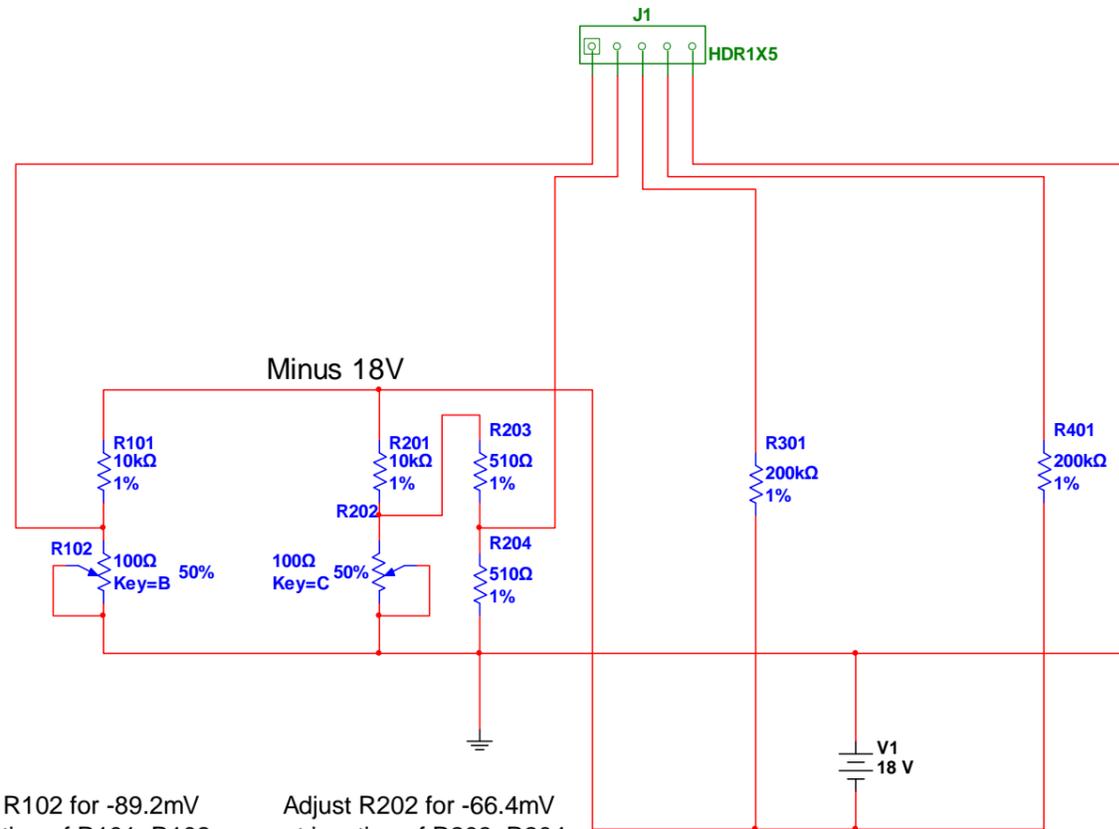Tektronix 015-0282-00 Levelling Head Substitute schematic
Revision 1.1 - 18th February 2009
Copyright © David C. Partridge, 2009



Adjust R102 for -89.2mV at junction of R101, R102 with the head attached.

Adjust R202 for -66.4mV at junction of R203, R204 with the head attached.

Adjustments of R102, R202 are one time adjustments to the calibration circuit.

The trim-pot shown as R7 in the levelling head schematic is used to calibrate the levelling head for variations in the forward voltages of the detector and reference diodes.

It allows the adjustment of the reference voltage at pin 4 over a range of just under 90mV.

When the levelling head is connected to an SG504, a bias current of 2.43uA is driven through the detector diodes and 87.3uA through the reference diodes, and -89.2mV is present at Pin1.

This circuit is designed to drive both the detector and reference diodes with the same current of 87.3uA.

R7 in the head is then adjusted for the same voltage on pins 3 and 4.

This is easiest to achieve by making a null measurement between Pin3 and Pin4.

With the original head attached, the voltage between Pin3 and Pin4 was less than 9mV without touching R7.

R7 in my original head was initially set exactly mid-range with -67.2mV at the wiper.

Adjustment for a "null reading" between Pin3 and Pin4 gave -75mV at the wiper, and -0.785V at Pin3 and Pin4. Varying the diode current by changing the supply voltage resulted in a differential voltage of +3mV at 50uA and -6mV at 150uA.

Refer to "Calibration Data.xls" for the details of the improvement in levelling after making this adjustment.